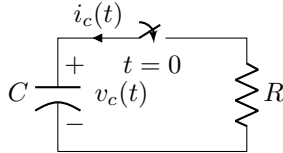


# Lecture 24, Mar 14, 2022

## Source-Free RC Circuits

- In a first-order transient circuit, the relationship between current and voltage can be described by a first-order differential equation
  - These are either RC or RL circuits (resistors and capacitors/inductors)
  - They can have sources or no sources
- Consider a source-free RC circuit:



- Suppose before time 0 the capacitor is energized to  $v_c(0^-) = V_0$ , and then at time 0, the switch is closed and the energizing circuit is removed
  - \* KVL gives:  $v_c(t) + Ri_c(t) = 0 \implies v_c(t) + RC \frac{dv_c}{dt} = 0 \implies v_c = -RC \frac{dv_c}{dt}$
  - \* This is a separable equation:  $\int \frac{1}{v_c} dv_c = \int -\frac{1}{RC} dt \implies \ln(v_c) + K = -\frac{t}{RC}$
  - \* Rearranging:  $v_c(t) = Ae^{-\frac{t}{RC}}$
  - \* Solving for initial conditions with  $v_c(0) = V_0$ , we obtain  $v_c(t) = V_0 e^{-\frac{t}{RC}}$ 
    - Note we can do this because a capacitor's voltage cannot change abruptly, so  $v_c(0^+) = v_c(0^-) = V_0$
    - We could not have started with current because we don't know the current at  $0^+$
  - \* The current is then  $i_c(t) = C \frac{dv_c}{dt} = -\frac{V_0 C}{RC} e^{-\frac{t}{RC}} = -\frac{V_0}{R} e^{-\frac{t}{RC}}$  or  $\frac{V_0}{R} e^{-\frac{t}{RC}}$  not following PSC
    - Note there is a discontinuity at time 0 as the current starts at 0 and jumps to  $\frac{V_0}{R}$ , and then decays to 0
- In a source-free RC circuit the voltage across the capacitor follows an exponential decay to 0
  - Large  $RC$  causes slower decay; small  $RC$  causes faster decay
  - Let  $\tau = RC$  be the *time constant* of the RC circuit;  $\tau$  characterizes how fast the voltage decays
  - $\tau$  can be found by finding the tangent at  $t = 0$ , and finding where the tangent intersects the horizontal axis
    - \*  $\frac{dv_c}{dt}(0) = -\frac{V_0}{RC}$  so tangent is  $y = V_0 - \frac{V_0 t}{RC}$ ; therefore when  $t = \tau = RC$  the tangent intersects the time axis
  - $\tau$  has the same unit as time (seconds), so that the argument of the exponential is unitless